

Arduino LED Controller Manual

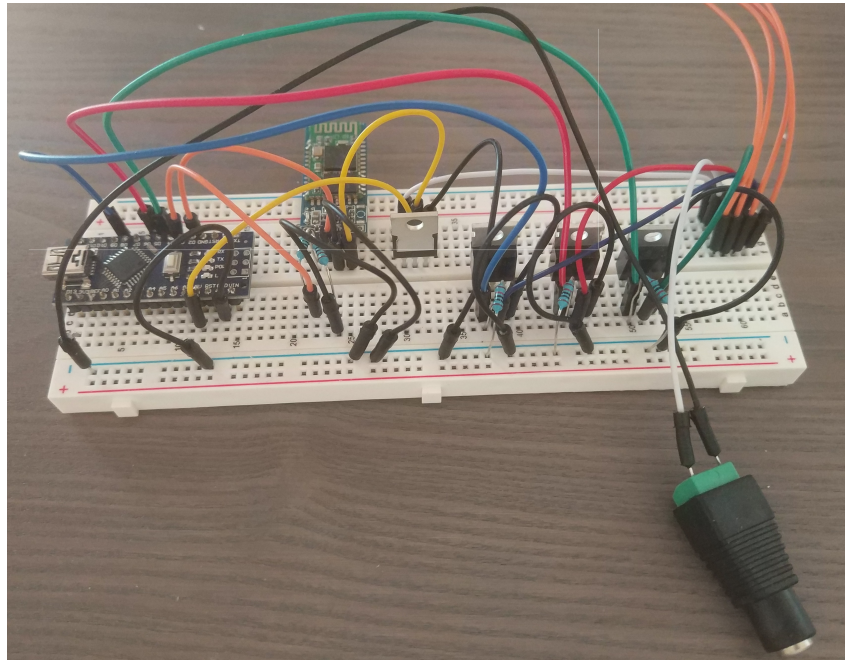


Figure 1: Breadboard Implementation

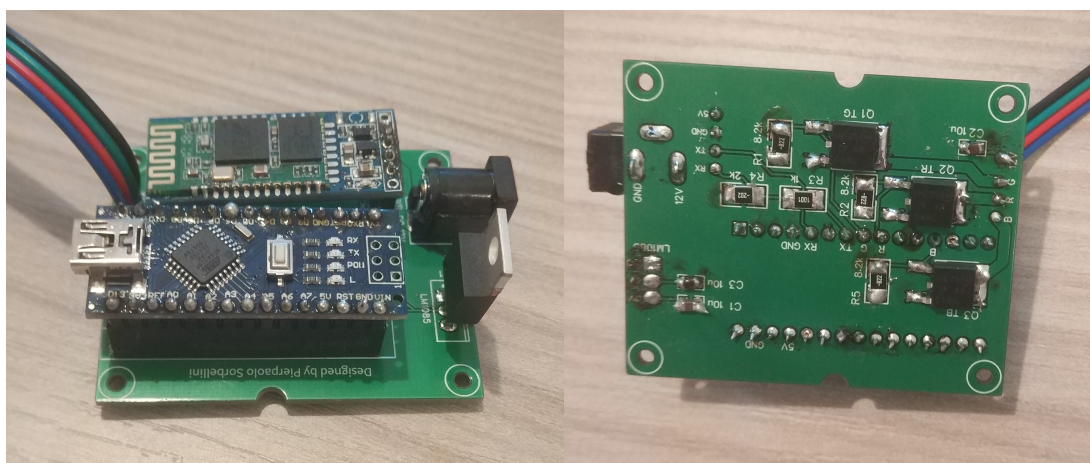


Figure 2: Welded PCB

Schematic and Components

The schematic of the controller circuit:

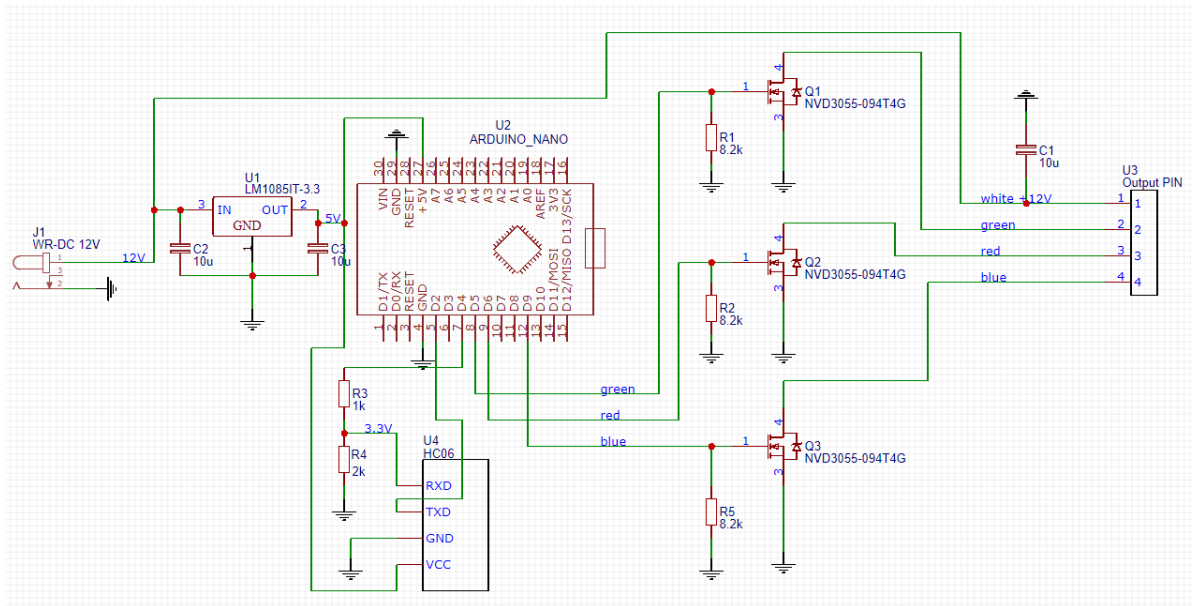


Figure 3: Schematic


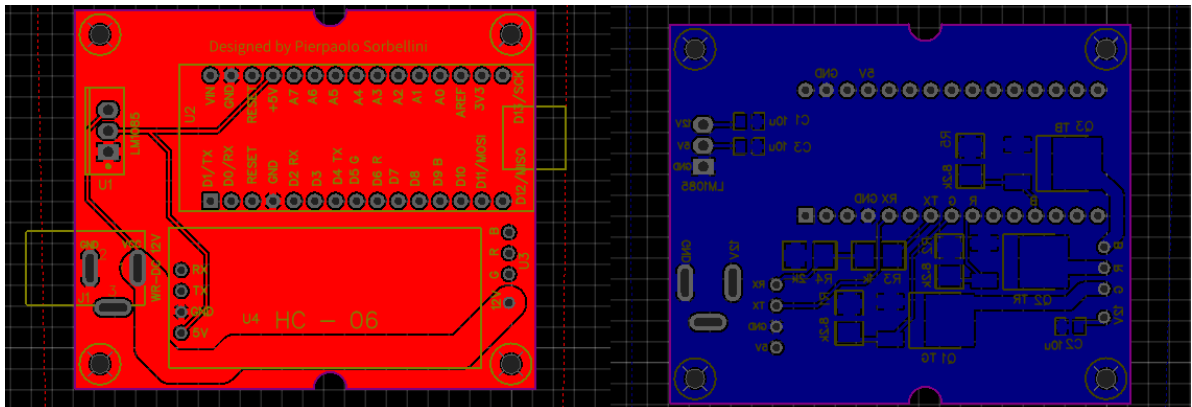



Figure 4: PCB Design

Specification on the components:

- 3x Transistor N-Channel that handle 2A at 12V, the package for the PCB implementation is DPAK (TO-252), 3 Pin. The transistor actually used are:
 - Breadboard: IRFZ44N
 - PCB: [NTD4804NT4G](#)
- Resistance package for PCB is 1210.
- Capacitor package for PCB is 0805.
- Voltage Regulator: [LM1085](#) package TO-220 also for the PCB implementation (improve thermal exchange)
- Bluetooth Module: HC-06.
- Arduino Nano
- Additional Component for PCB connectivity:
 - [1x12V-Socket](#)
 - 1x RGB connector

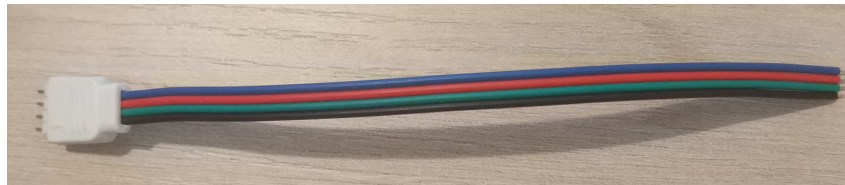

- 3x 15Pin Socket

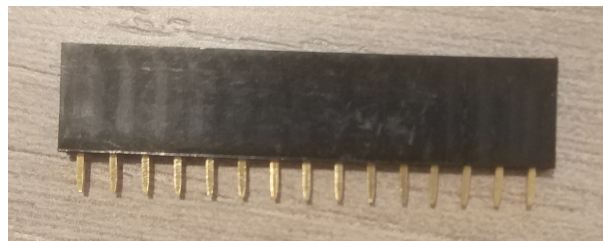

2 of them are needed for the arduino nano to be connected with the PCB and the third one is cut to get a 4pin Socket to connected the Bluetooth module.

Download and Setting Procedure

Once the circuit is composed:

- Upload the script on the Arduino.
- Download the App to connect to the bluetooth module and run it.

Download:

- [Arduino-Script](#)
- [Case-for-3D-printing](#)
- [Gerber-for-PCB](#)